

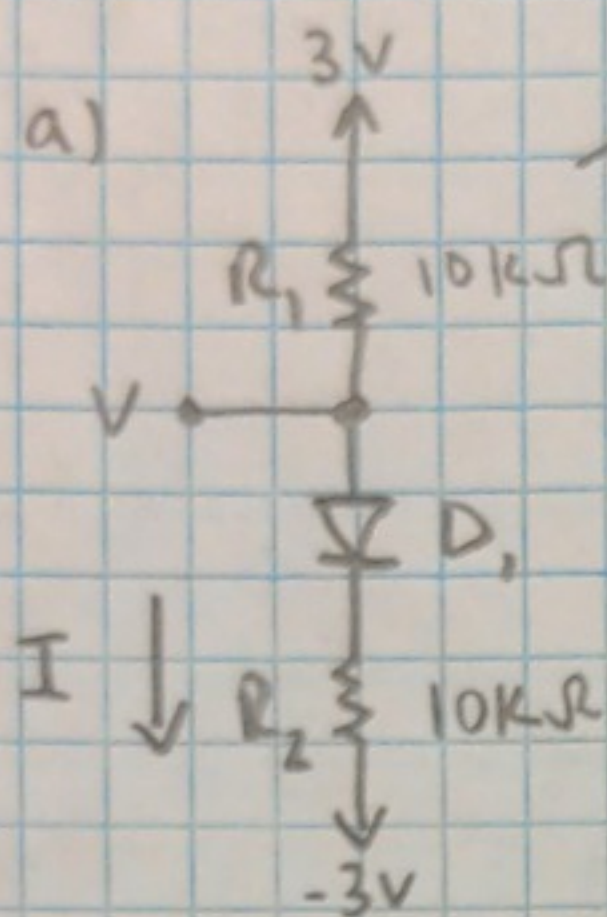


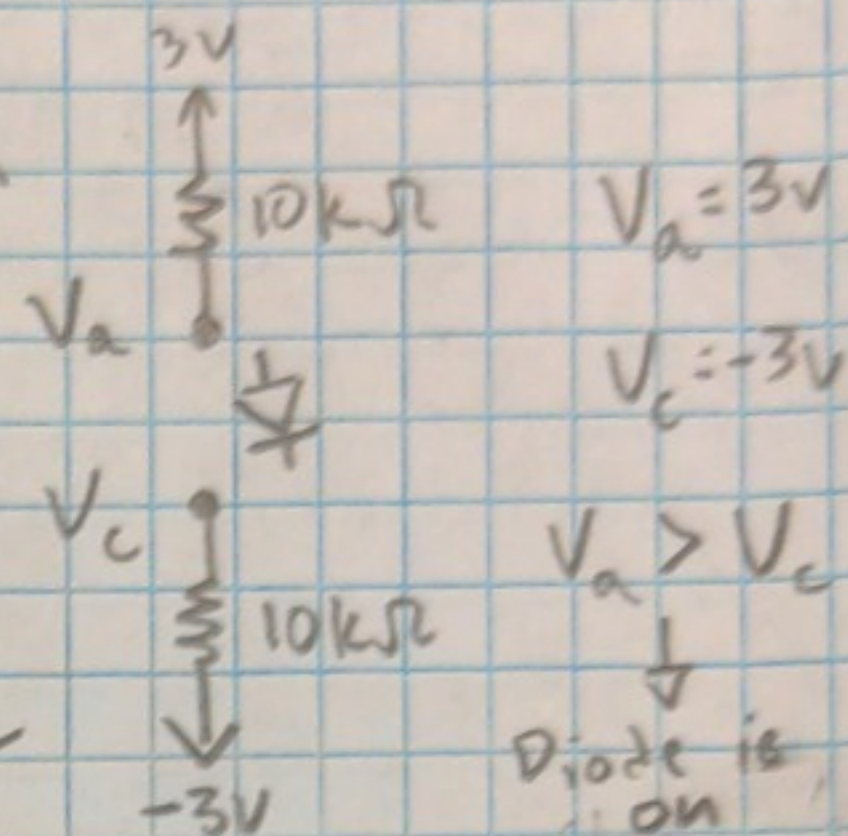1. Assuming the diodes are ideal, calculate I, V in the following circuits.



Assume Diode is off:

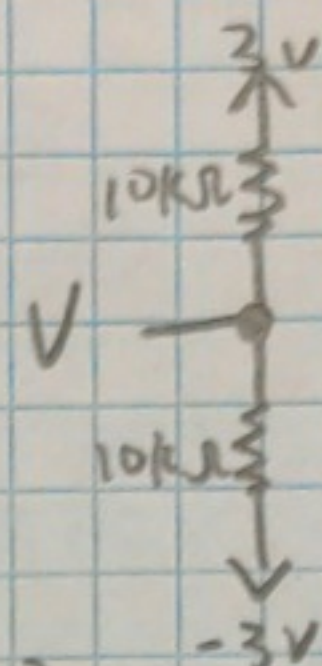


$$I = \frac{3V - (-3V)}{10k\Omega + 10k\Omega}$$

$$V = 3V - IR_1$$



$$V = 3V - (.3mA)(10k\Omega)$$

$$I = \frac{6V}{20k\Omega}$$

a: $I = .3mA$ $V = 0V$

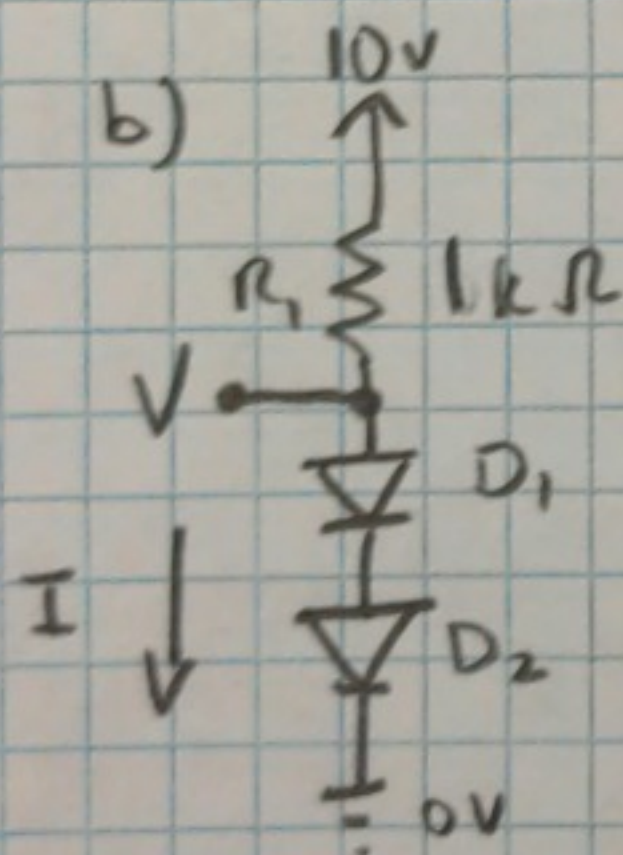

Assume Diodes are off:

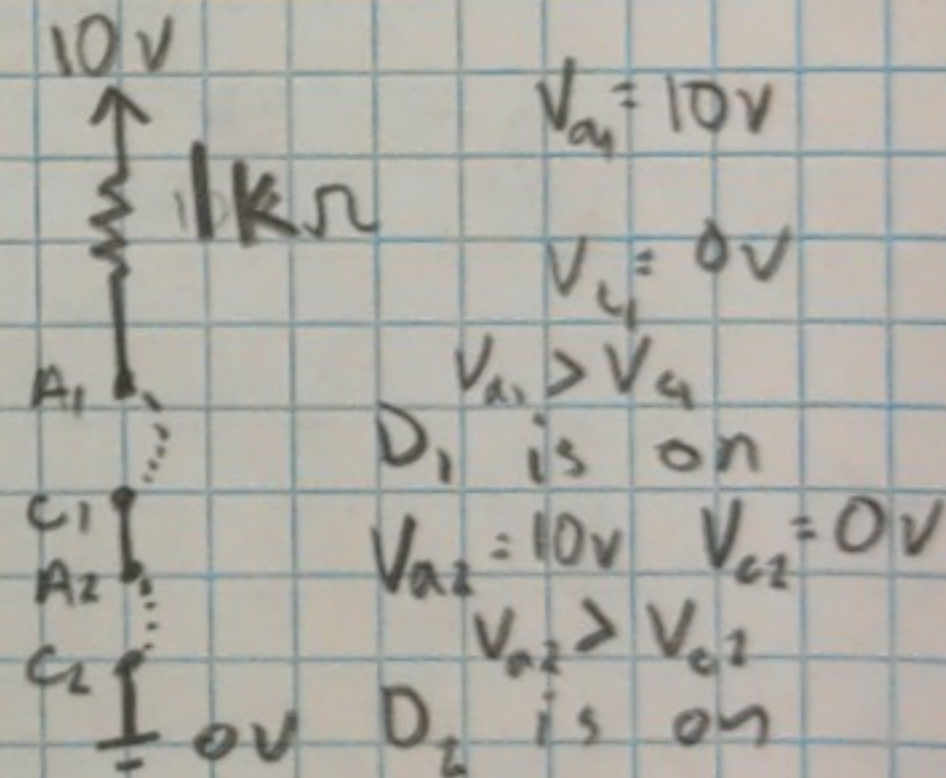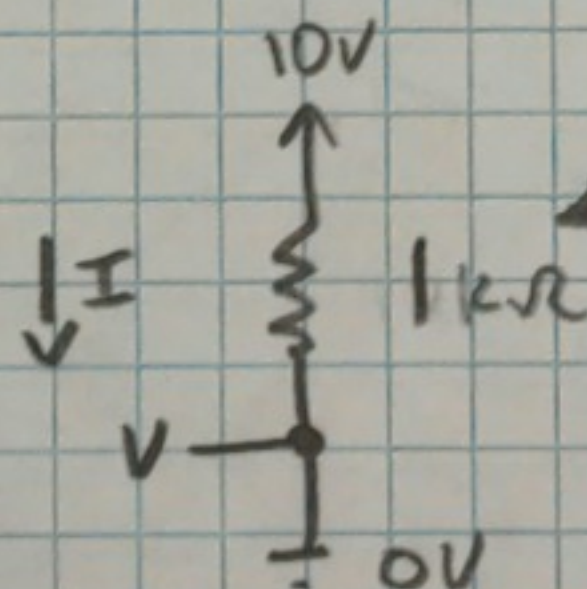


$$V = 0V$$



$$I = \frac{10V - 0V}{1k\Omega}$$

b: $V = 0V$ $I = 10mA$

b. c)

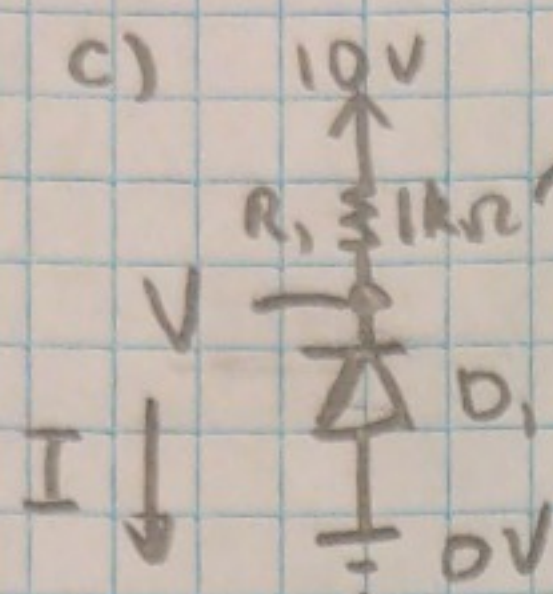


Assume Diode is off:

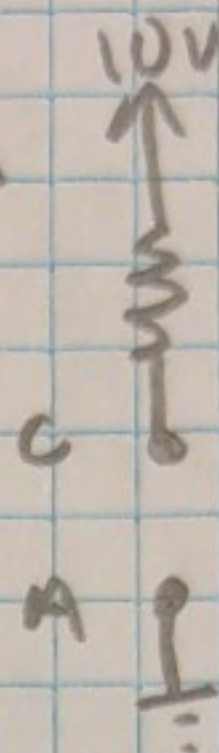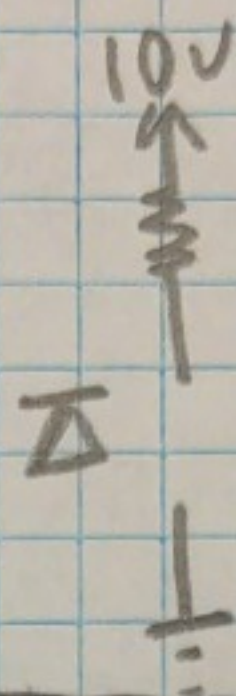



$V_a = 0V$
 $V_c = 10V$
 $V_c > V_a$
 Diode is off

c: $V = 10V$ $I = 0A$

d)

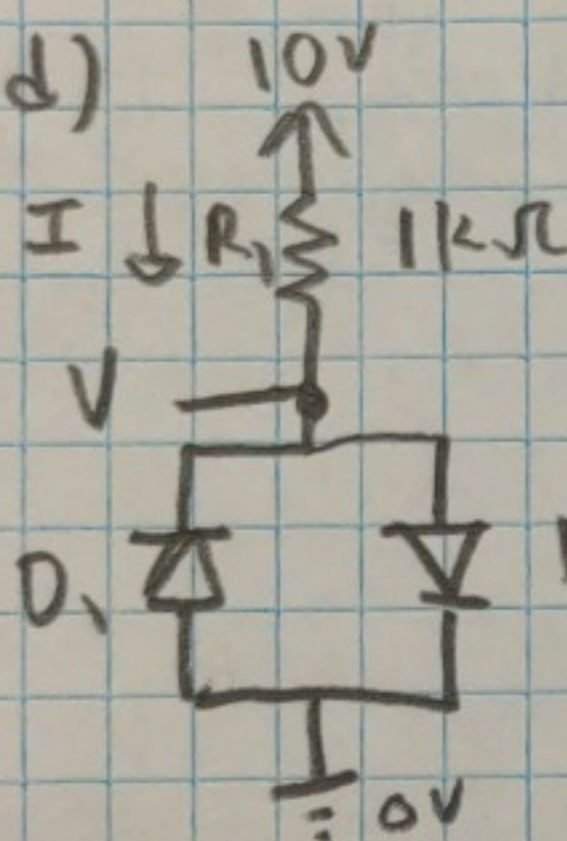

Assume Diodes are off:

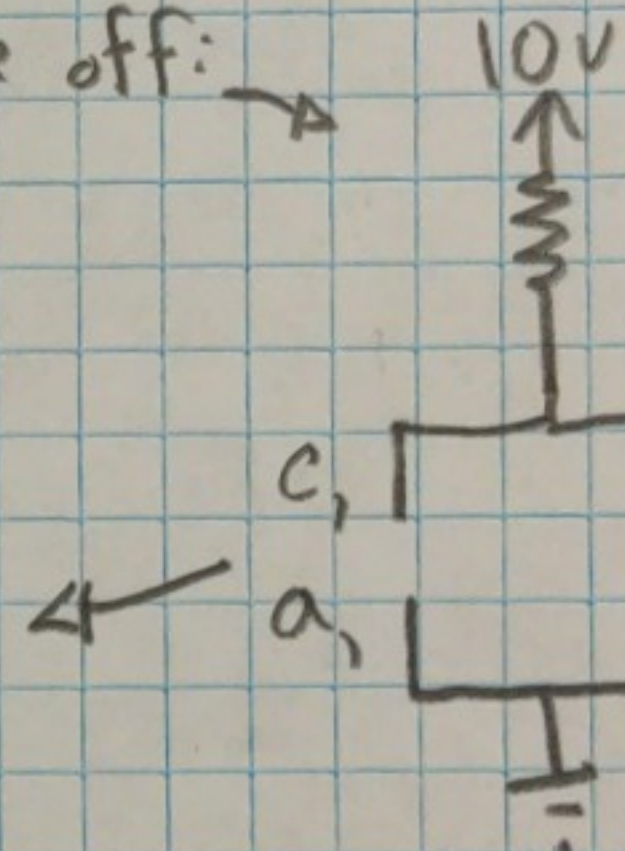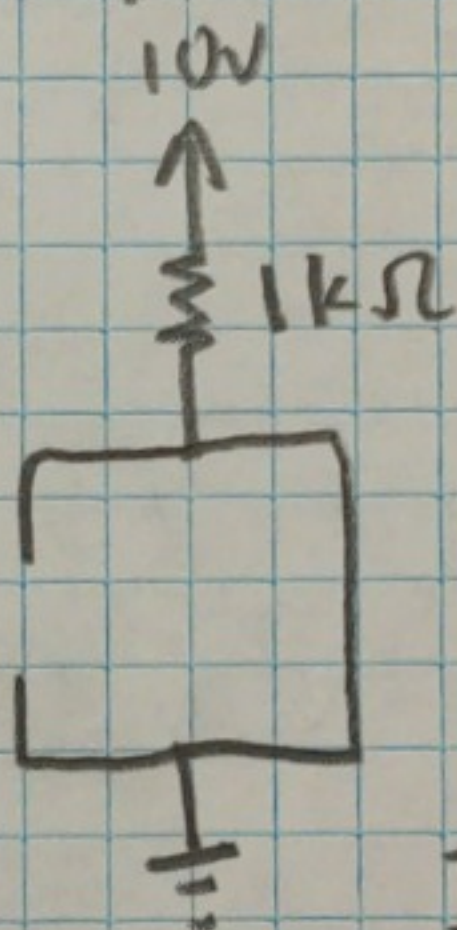

$V_{C1} = 10V = V_{A1}$
 $V_{A1} = 0V = V_{C2}$
 D_1 is off
 D_2 is on

$$I = \frac{10V - 0V}{1k\Omega}$$

d: $V = 0V$ $I = 10mA$

2. Assuming the diodes are ideal, calculate I, V in the following circuits

a) $10V$
 $R_1 = 10k\Omega$
 D_1 (anode to $0V$)
 D_2 (anode to $-V$)
 $R_2 = 6k\Omega$
 I (current through R_2)
 $-10V$

Assume Diodes are on: \rightarrow

V_a would have to be $0V$
 $i_1 = \frac{10V - 0V}{10k\Omega} = 1mA$
 $i_3 = \frac{0V - (-10V)}{6k\Omega} = 1.66mA$

KCL @ a): $i_1 = i_2 + i_3$
 $i_2 = i_1 - i_3 \rightarrow i_2 = 1mA - 1.66mA$
 $i_2 = -.66mA$ not possible

D_1 off, D_2 on? \triangleleft

$V_{a1} = 10V - IR_1$
 $V_{a1} = -2.5V$
 $V_{a1} < V_{c1}$
 Diode is still off

$I = \frac{10V - (-10V)}{16k\Omega} = 1.25mA$

This works!

$V = -2.5V$
 $I = 1.25mA$



Chris Hunt

HW1

ECE322

2. b)

Assume diodes are off;

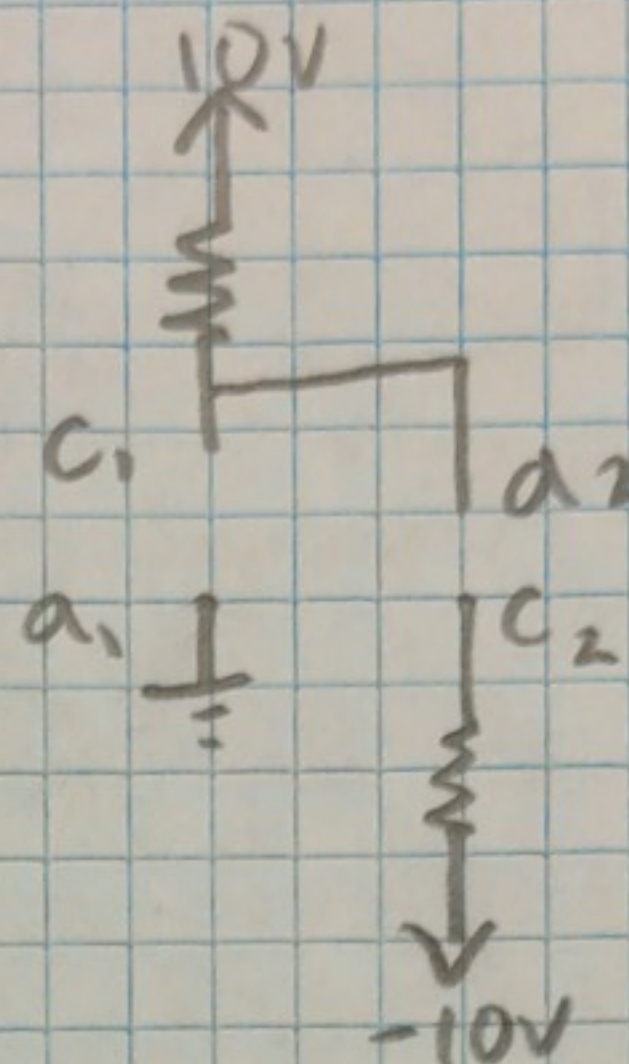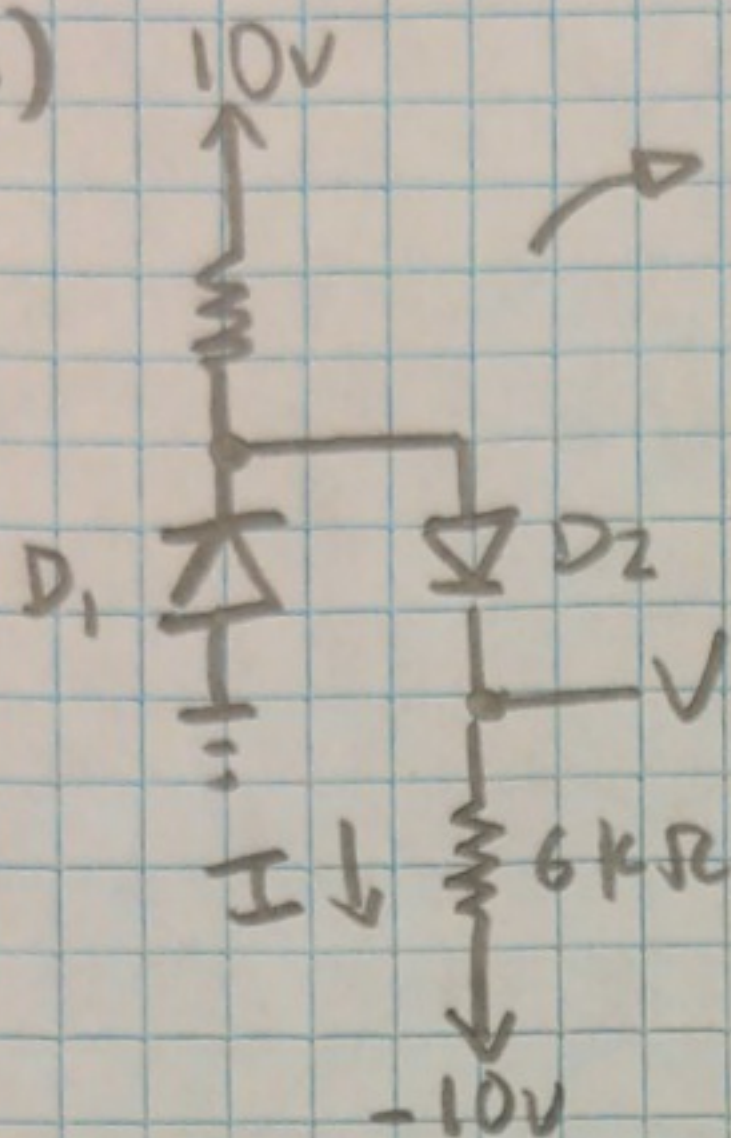

$$V_{c1} = V_{a2} = 10V$$

$$V_{a1} = 0V$$

$$V_{c2} = -10V$$


$$D_1) V_{a1} < V_{c1}$$

D₁ is off

$$D_2) V_{a2} > V_{c2}$$

D₂ is on

Test it

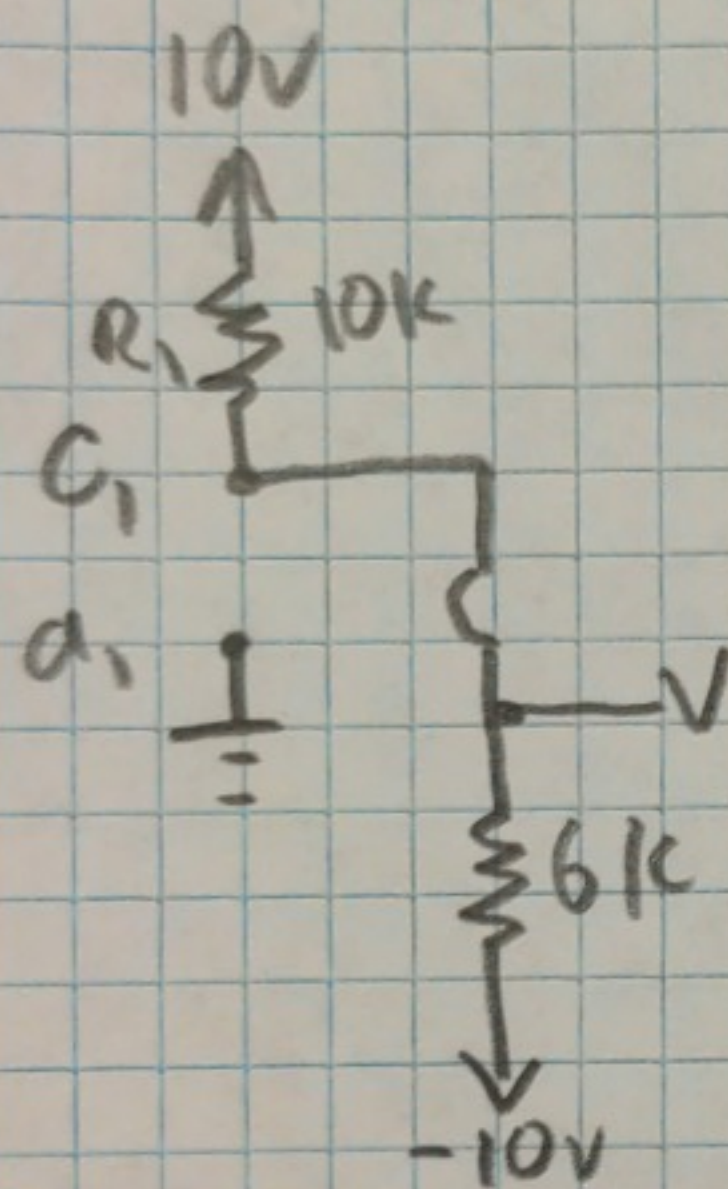

$$V_{c1} = 10V - IR_1$$

$$V_{c1} = -2.5V$$

$$V_{a1} = 0V$$

$$V_{a1} > V_{c1}$$

D₁ is on

$$I = \frac{(10V - (-10V))}{16k\Omega} = 1.25mA$$

$$V_a = 0V = V$$

$$KCL @ a) I = i_1 + i_2$$

$$I = \frac{0 - (-10V)}{6k\Omega} = 1.67mA$$


$$i_1 = \frac{10V}{10k\Omega} = 1mA$$

$$1.67mA = 1mA + i_2$$


$$i_2 = .67mA$$

$$V = 0$$


$$I = 1.67mA$$

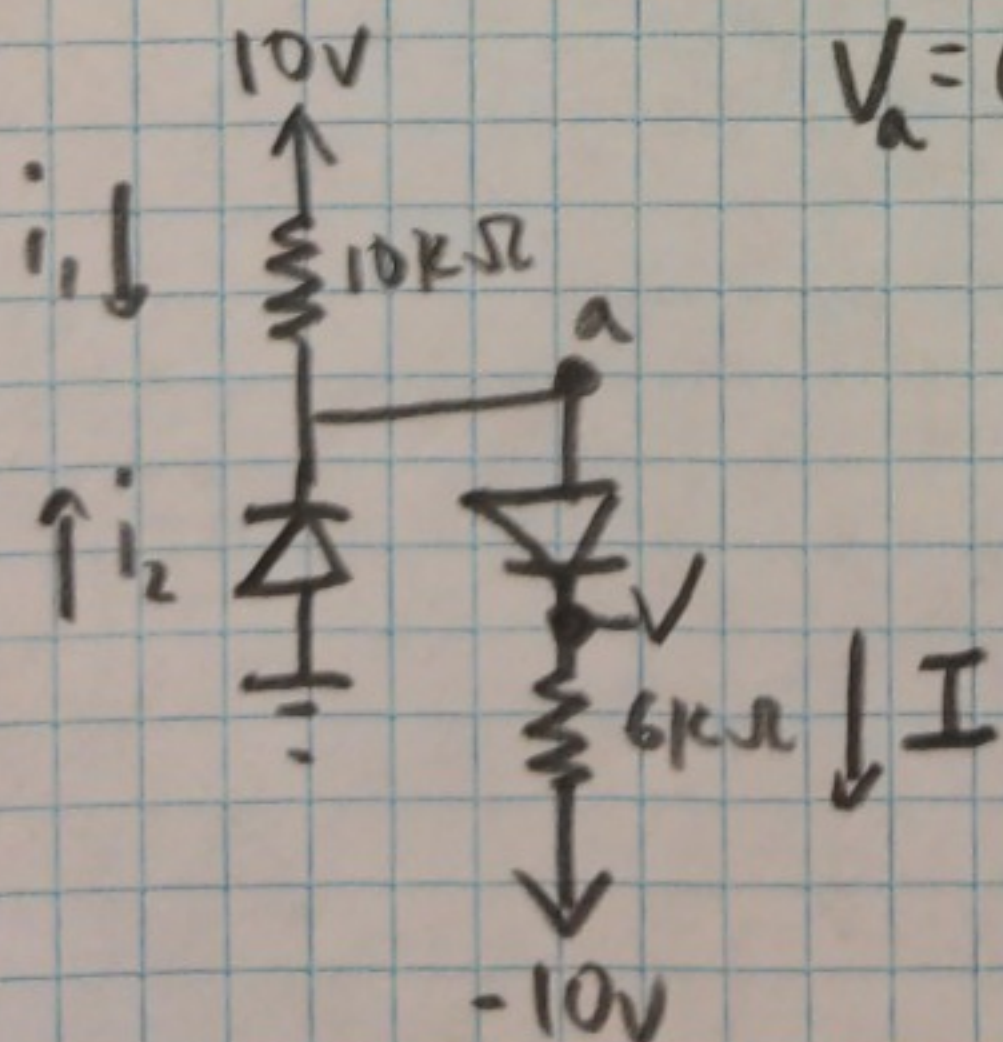

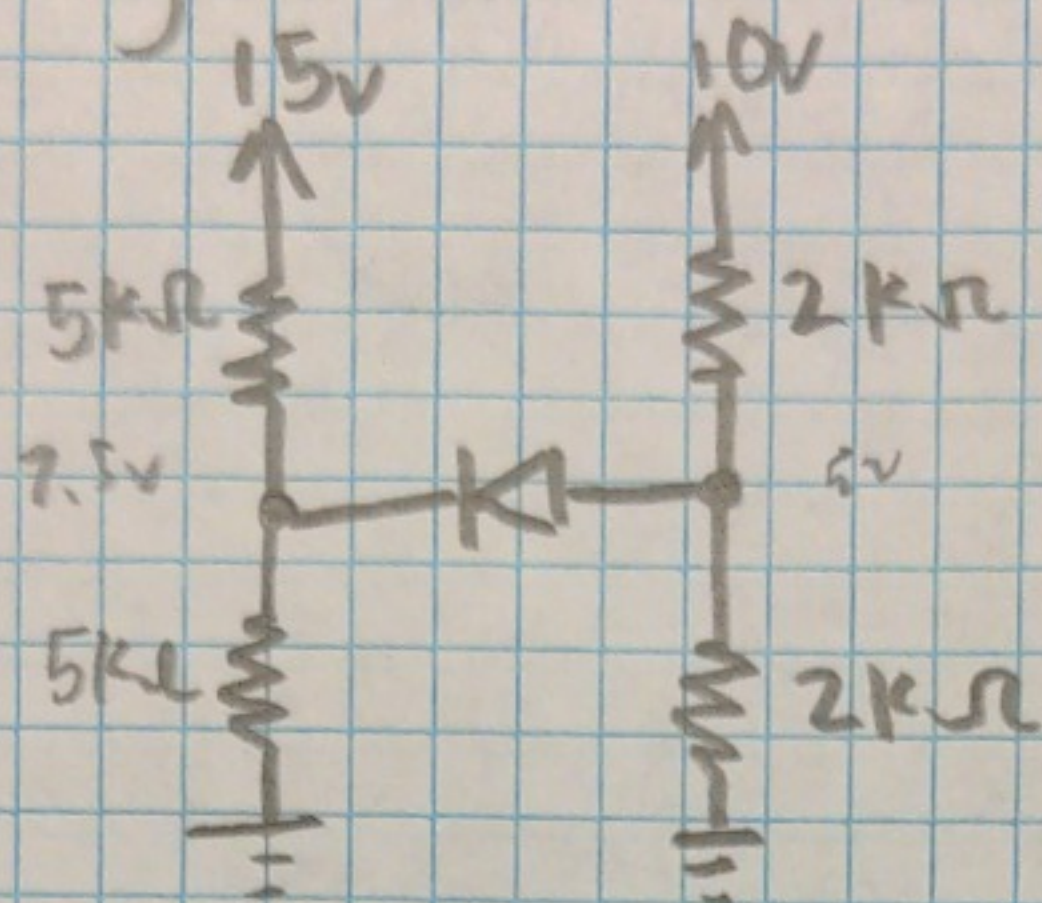3. Assuming the diodes are ideal, use thevenin's theorem to simplify the circuit and find V, I




Left side Thevenin Equivalent:

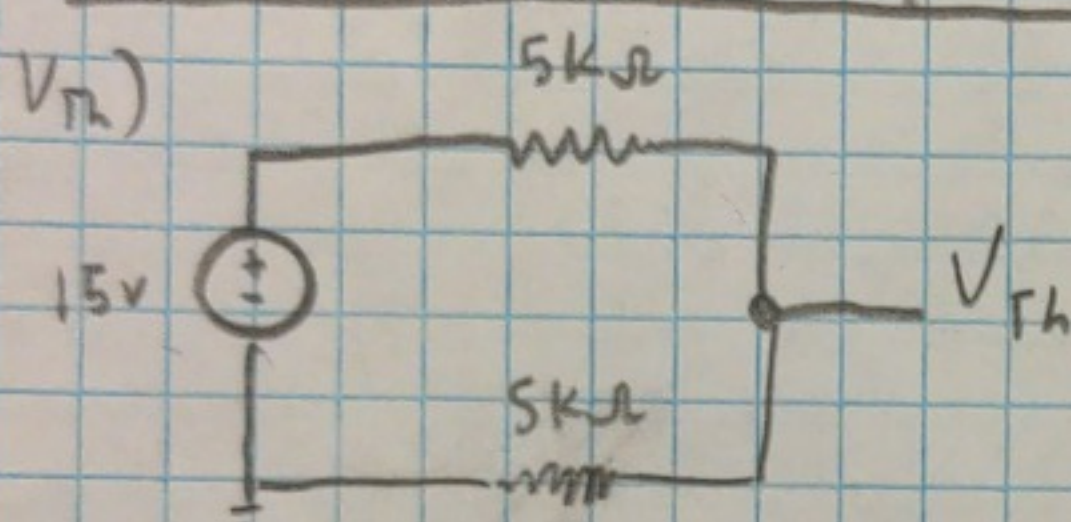

$$V_{Th} = 15V \left(\frac{5k}{10k} \right)$$


$$V_{Th} = 7.5V$$

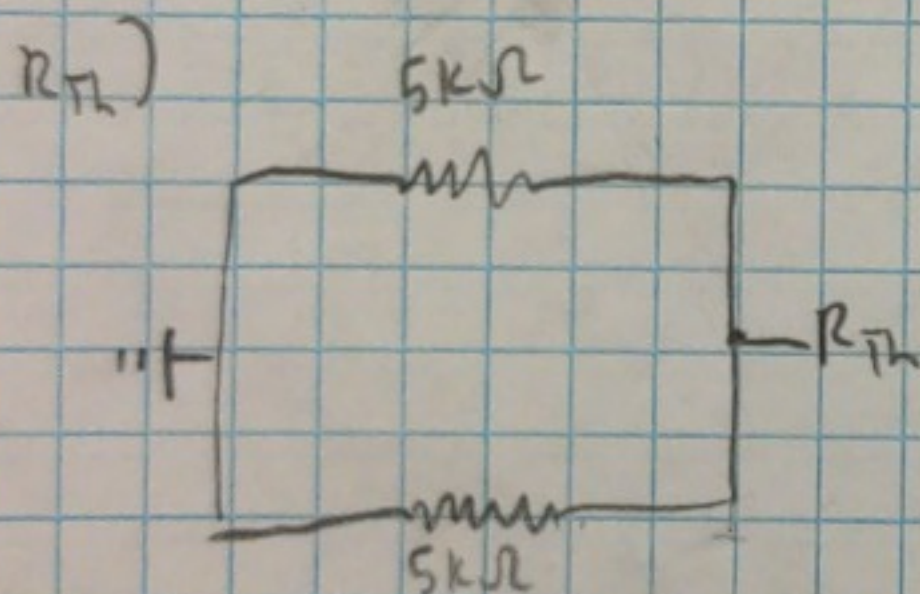

$$R_{Th} = 5k\Omega \parallel 5k\Omega$$


$$R_{Th} = 2.5k\Omega$$

Right side Thevenin Equivalent:

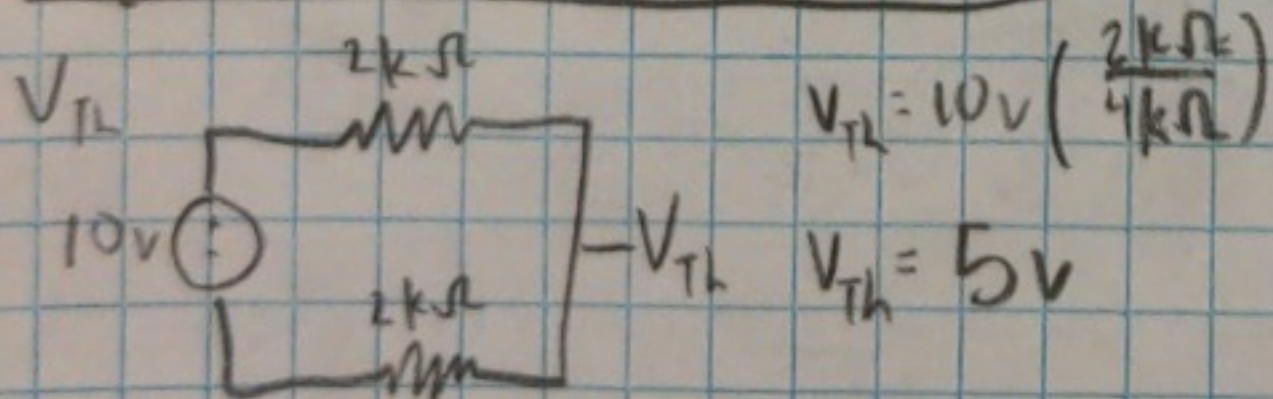


$$V_{Th} = 10V \left(\frac{2k}{4k} \right)$$

$$V_{Th} = 5V$$

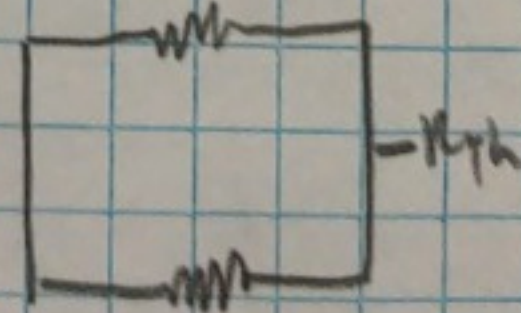

$$R_{Th} = 2k\Omega \parallel 2k\Omega$$

$$R_{Th} = 1k\Omega$$

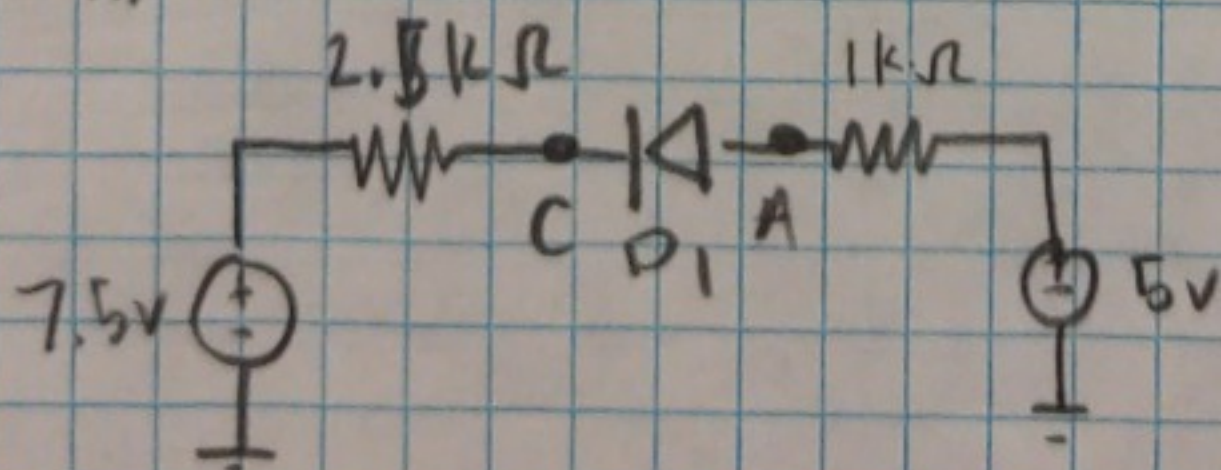

Assume D_1 is off:

$$V_C = 7.5V \quad V_A = 5V$$

$$V_A < V_C$$

D_1 is off
no current

$$V = 5V - 7.5V = -2.5V$$

$$I = 0A$$

4. A diode is conducting in Forward bias region with a current of 1mA and $V_d = 0.7V$. If the current is changed to 10mA, what is V_d ?

$$V_{th} = 25mV$$

$$I_d = I_s (e^{V_d/nV_{th}} - 1)$$

First Find I_s

$$1mA = I_s (e^{0.7/0.025} - 1) \rightarrow I_s = \frac{0.001}{e^{0.7/0.025} - 1}$$

$$I_s = 6.91 \times 10^{-16}$$

Find V_d

$$I = 10mA \quad I_s = 6.91 \times 10^{-16} \quad V_{th} = 25mV$$

$$I = I_s (e^{V_d/nV_{th}} - 1)$$

$$\frac{I}{I_s} + 1 = e^{V_d/nV_{th}}$$

$$\ln\left(\frac{I}{I_s} + 1\right) = \frac{V_d}{nV_{th}}$$

$$nV_{th} \ln\left(\frac{I}{I_s} + 1\right) = V_d$$

$$V_d = 0.025 \ln\left(\frac{0.01}{6.91 \times 10^{-16}} + 1\right)$$

$$V_d = 0.757V$$


Chris Hunt

HW1

ECE 322

5. Assuming the constant voltage drop model ($V_D = 0.7V$)
Calculate V, I



a)

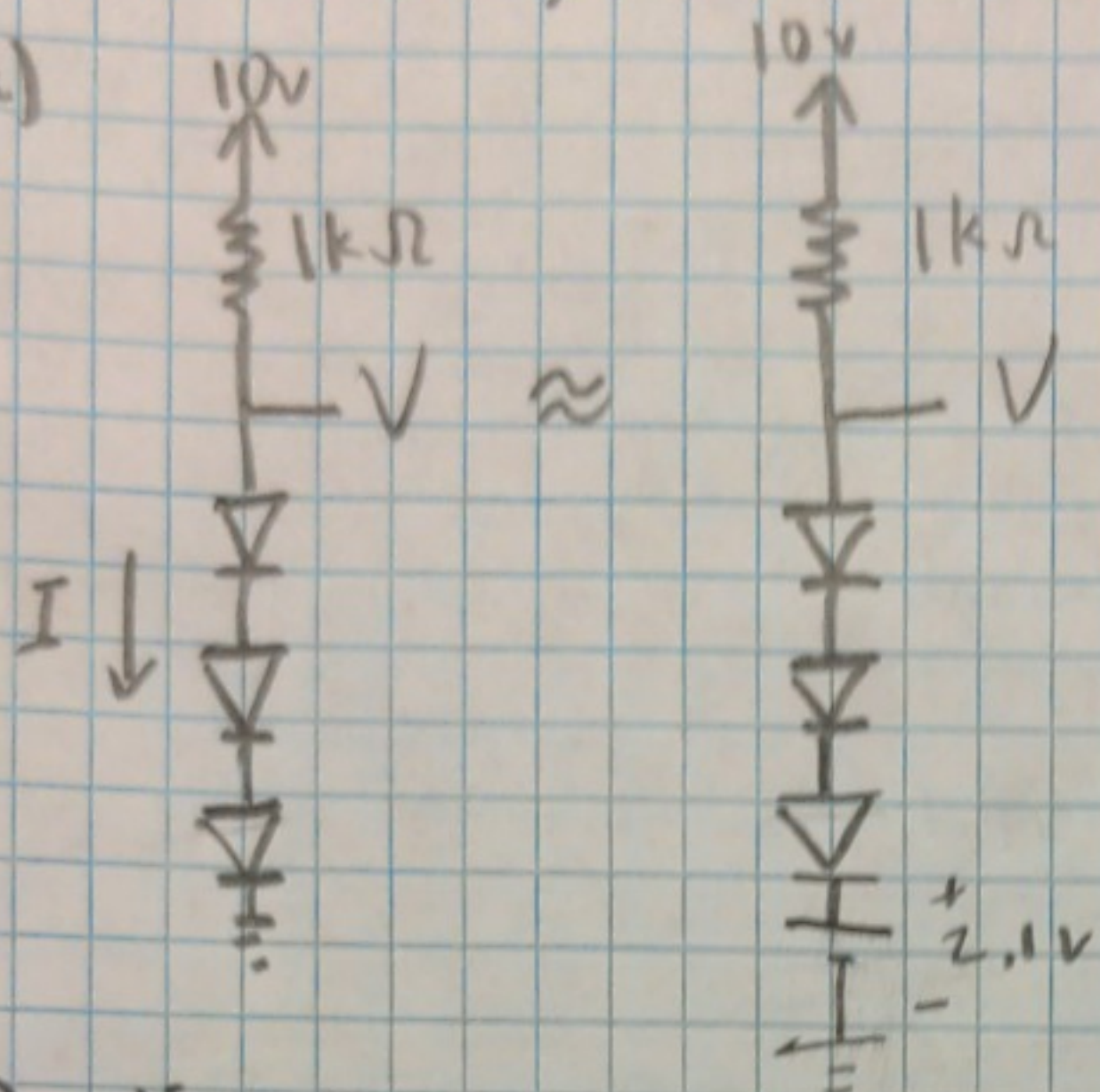

$$V = 2.1V$$

$$I = \frac{10V - 2.1V}{1k\Omega} = 7.9mA$$

b)

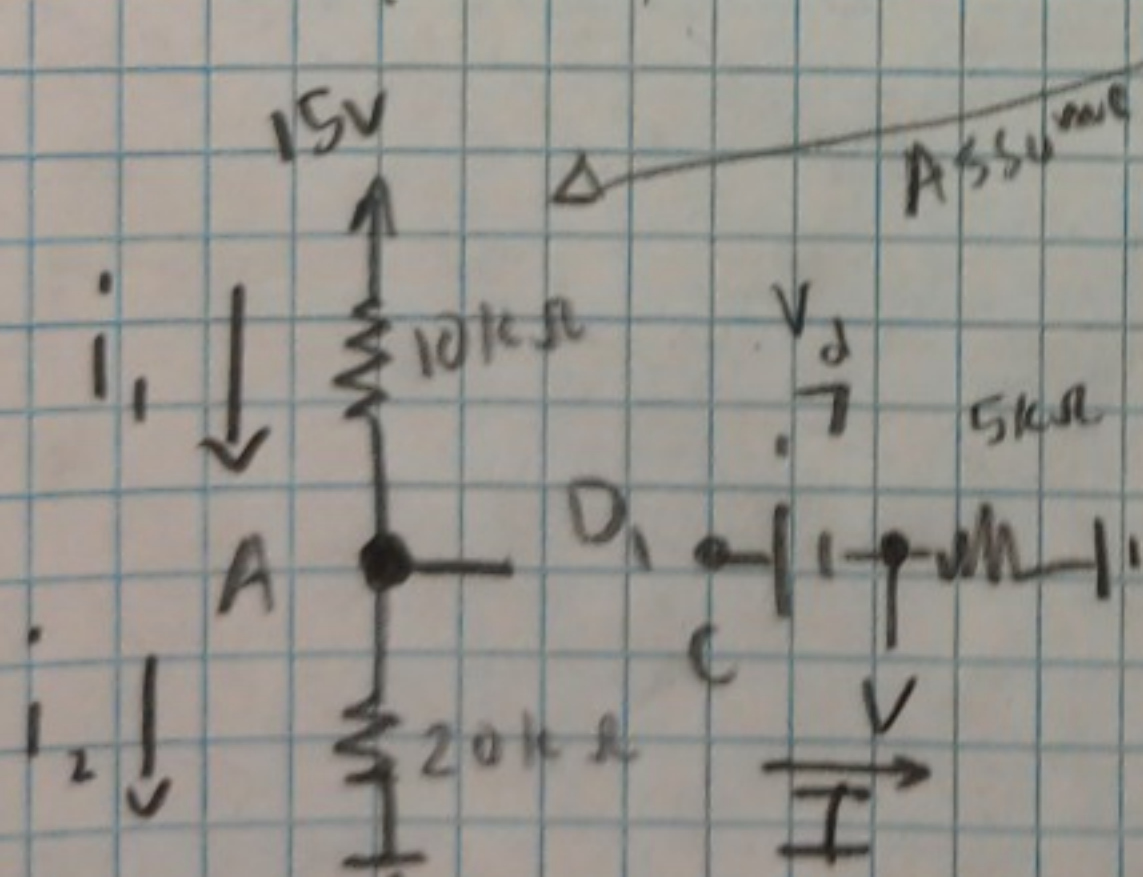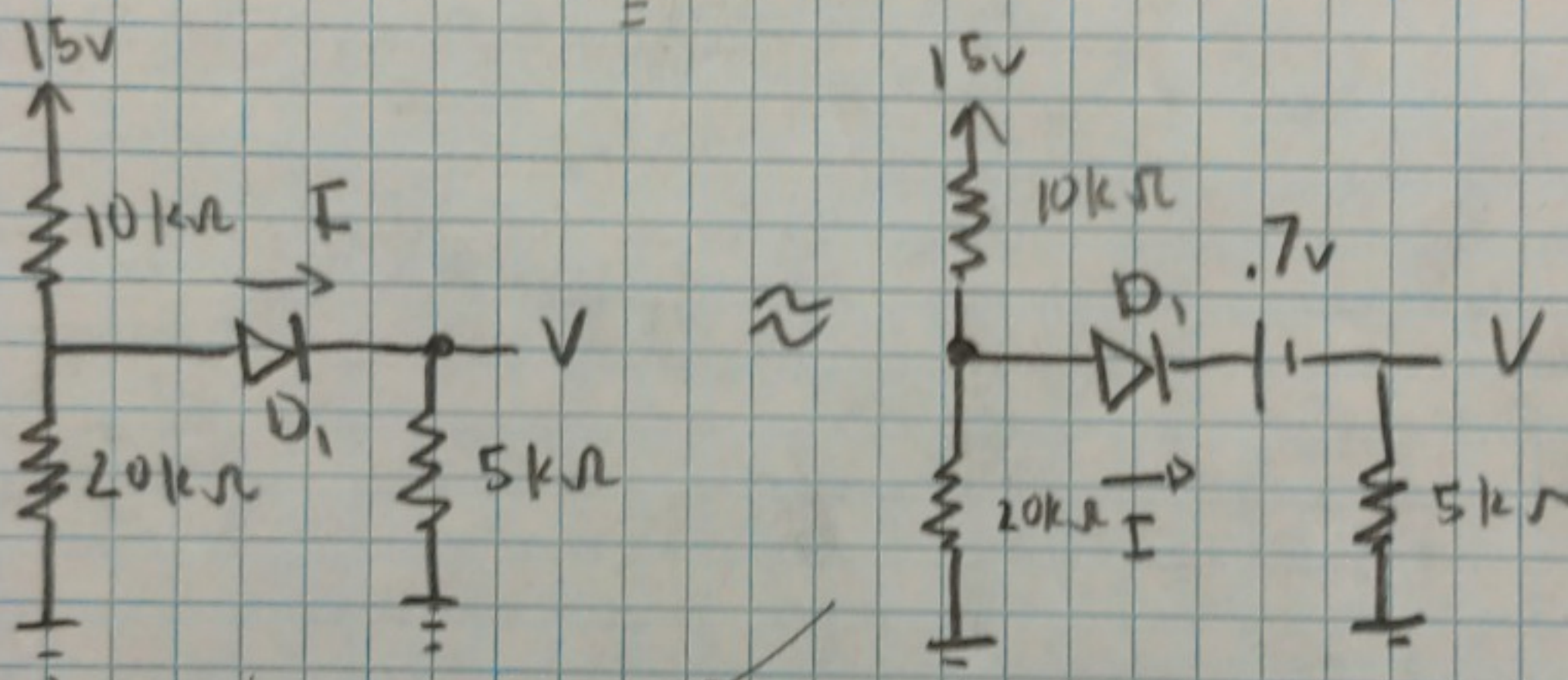

Assume off

$$V_a = 15V \left(\frac{20k\Omega}{30k\Omega} \right) = 10V$$

$$V_c = 0.7V \quad V_a > V_c \quad D_1 \text{ is on}$$

$$KCL @ A) \quad i_1 = i_2 + I$$

$$\frac{15V - V_a}{10k\Omega} = \frac{V_a}{20k\Omega} + \frac{V_a - 0.7V}{5k\Omega}$$

$$V = V_a - 0.7V$$

$$V = 3.98V$$


$$I = \frac{3.98V}{5k\Omega} = 0.797mA$$

$$30V - 2V_a = V_a + 4V_a - 2.8V$$


$$7V_a = 32.8V$$

$$V_a = 4.69V$$

6.

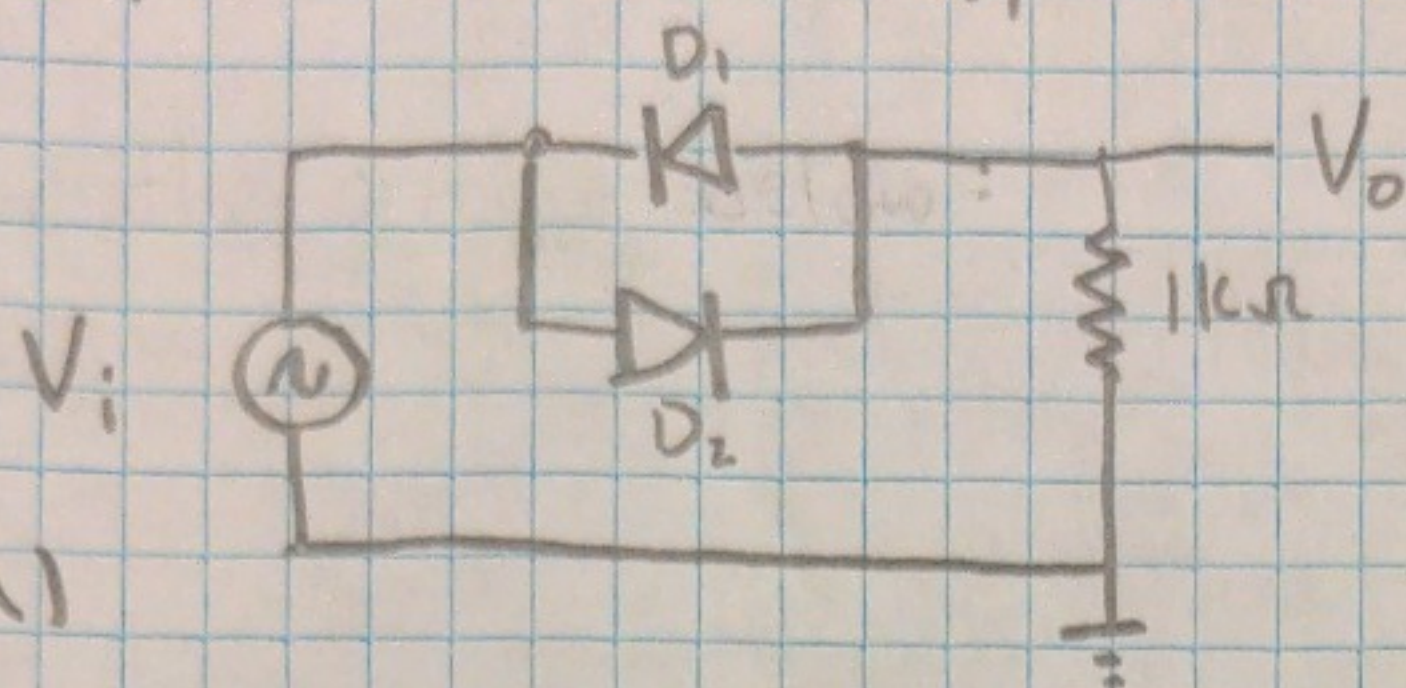
Assume $V_D = 0.7\text{V}$

$$V_i = 10 \sin(\omega t)$$

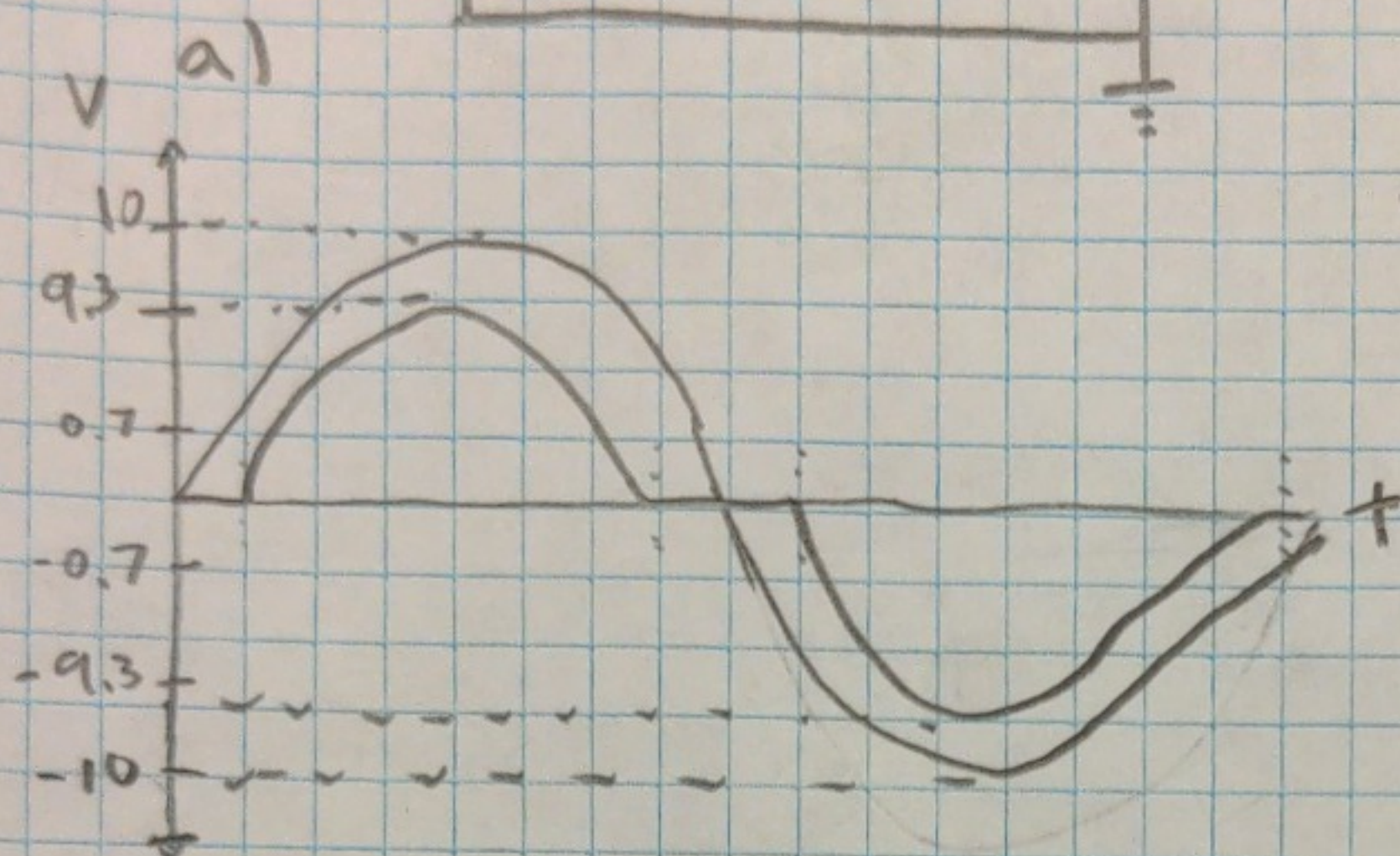

There are 3 distinct regions of V_i that determine V_o .

- | | | | |
|------|--------------------|-----------|-----------|
| I: | $V_i > 0.7$ | D_1 OFF | D_2 ON |
| II: | $V_i < -0.7$ | D_1 ON | D_2 OFF |
| III: | $-0.7 < V_i < 0.7$ | D_1 OFF | D_2 OFF |

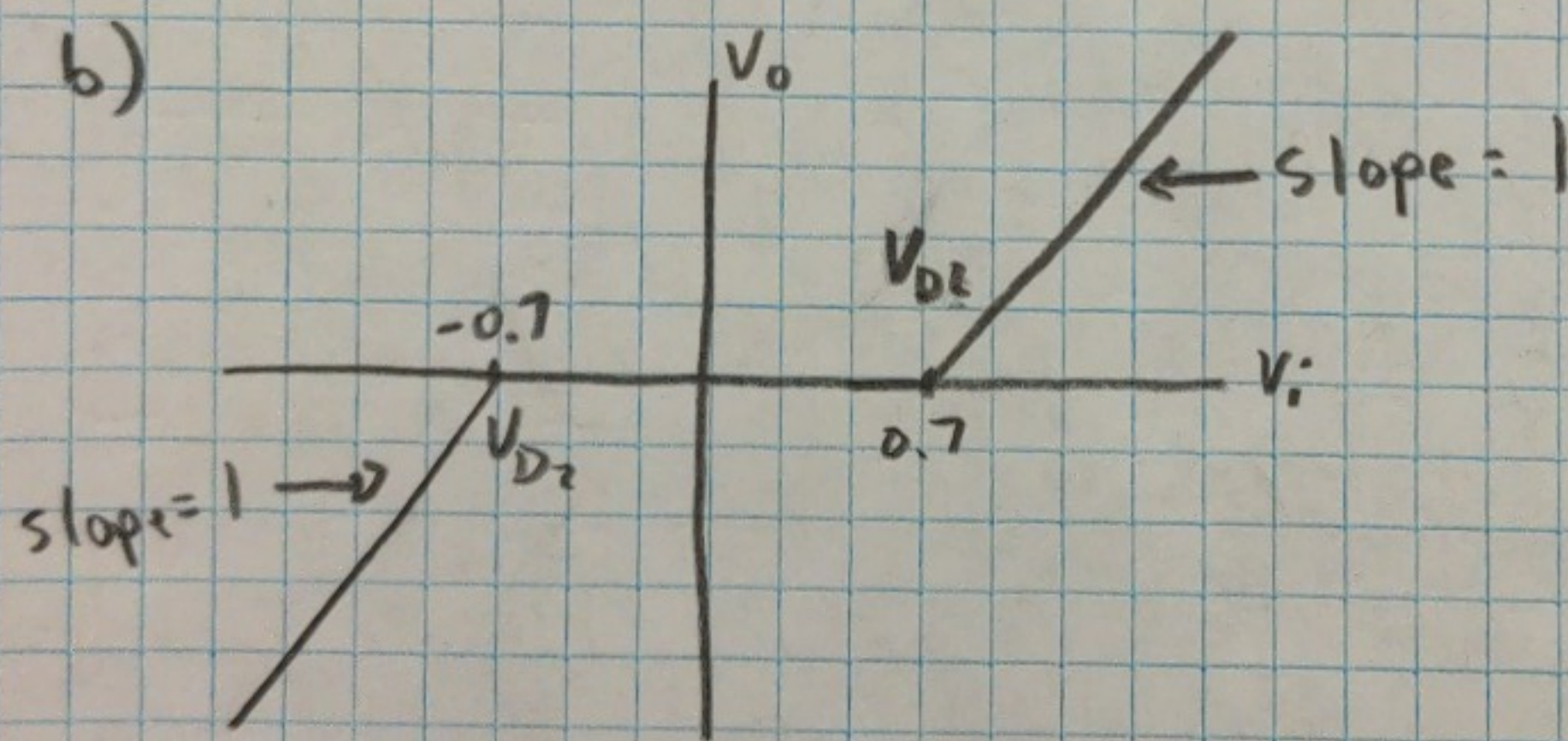

c) What is the average value of V_o ?

The waveform retains the symmetry of V_i .
The average value of V_o is therefore 0.