

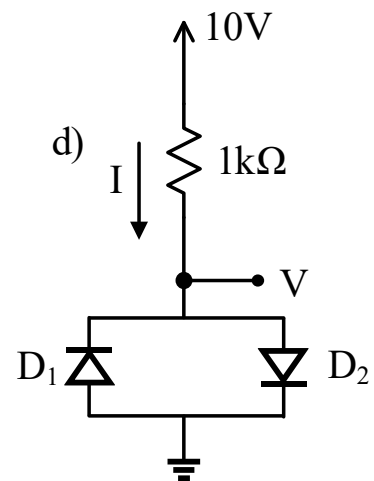
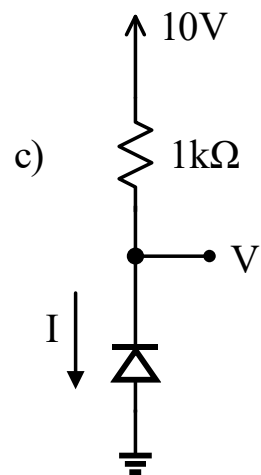
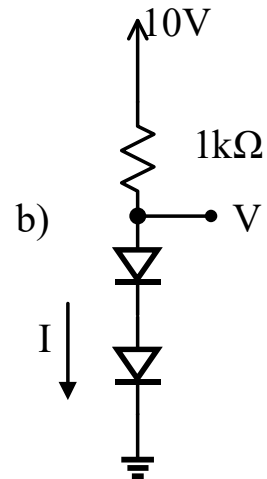


ECE 322 HW#1

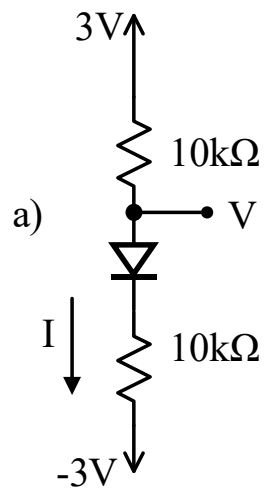
1. Assuming the diodes are ideal, calculate I, V in the following circuits



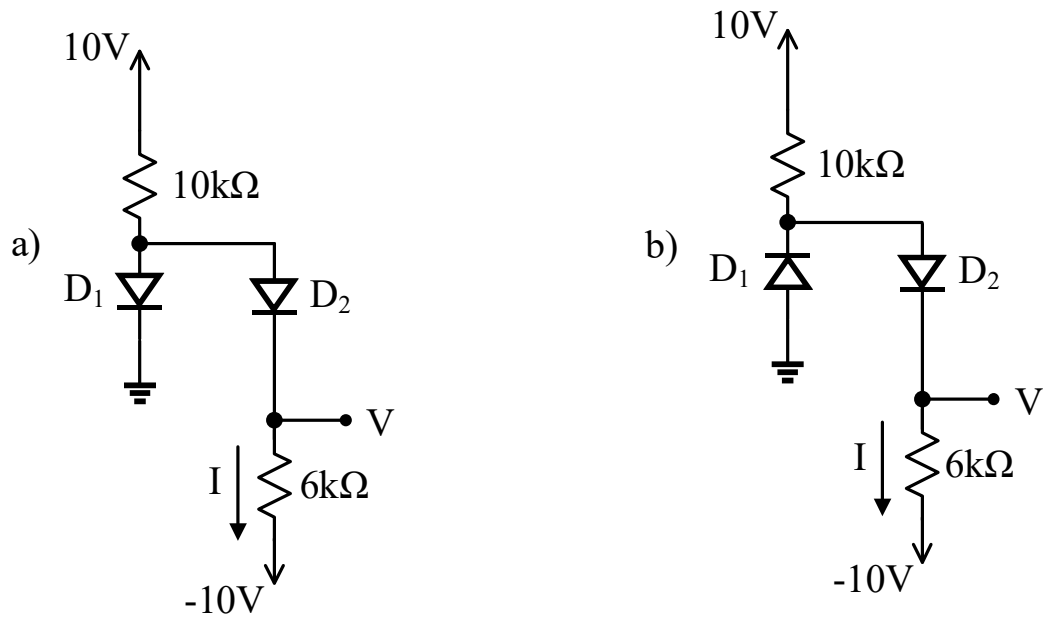2. Assuming the diodes are ideal, calculate I, V in the following circuits





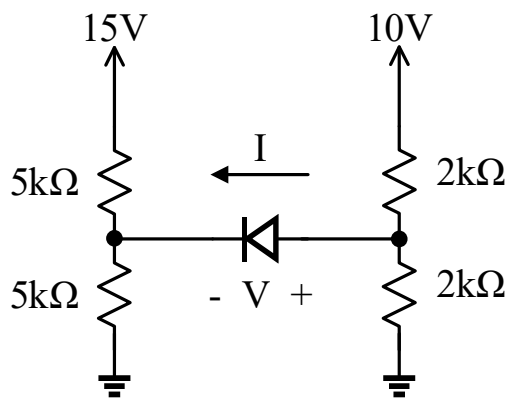3. Assuming the diodes are ideal, use thevenin's theorem to simplify the circuit and find V & I




4. Assume real diode model in this question ($V_{th}=25\text{mV}$). A diode is conducting in forward bias region with a current of 1mA and voltage across the diode is 0.7V . If the current is changed to 10mA , what is the new voltage across the diode?

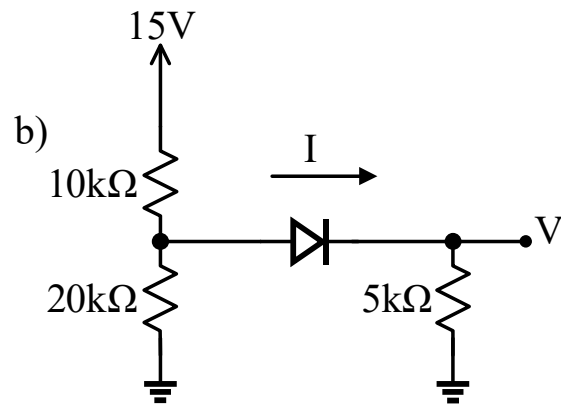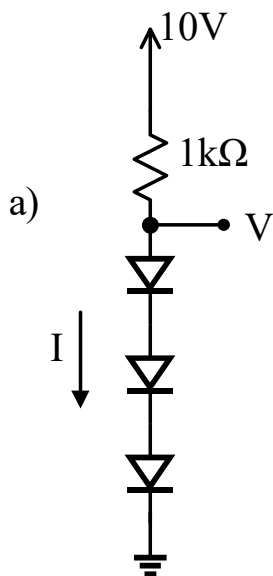5. Assuming the constant voltage drop model ($V_D=0.7\text{V}$), Calculate V & I in the following circuits.



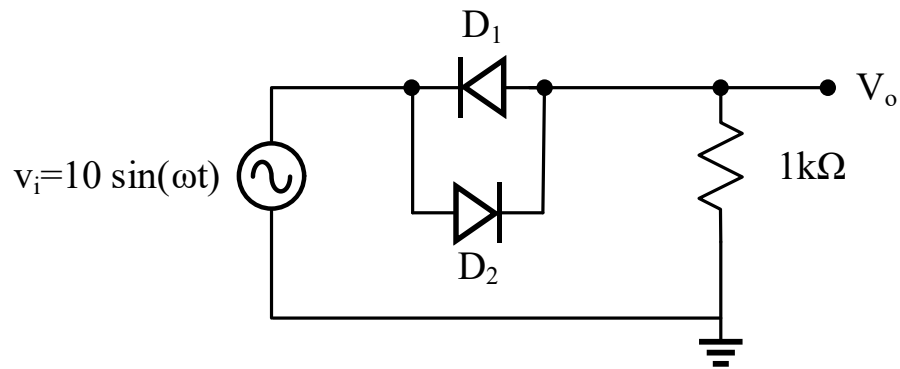6. For the circuit shown below answer the following questions: (assume constant voltage drop model $V_D = 0.7$)



- Sketch the waveform V_o .
- Draw the input output characteristics.
- What is the average value of V_o ?